

EE 5193 — FPGA and HDL

Summer 2026

Electrical and Computer Engineering Department

University of Texas at San Antonio

A Multi-Cycle 16-Bit RISC Processor on the Nexys A7

Course Project Report

Sergio Arreola

July 10, 2026

Table of Contents

2. Problem Statement.....	4
3. Approach.....	4
3.1 Multi-cycle organization	4
3.2 One unified memory	5
3.3 Controller	5
3.4 Reuse of previously developed modules	6
3.5 Register file and instruction formats	6
3.6 Initial data and hand-calculated results.....	6
3.7 Clocking, reset, and the display path	7
4. Block Diagram	7
5. ASM-D Charts.....	8
5.1 Overall four-step loop	8
5.2 Execute-step branching per opcode	9
6. Controller Output Table.....	10
7. Verilog Code.....	10
7.1 controller.v — the FSM controller	11
7.2 pc.v — program counter	14
7.3 ir.v — instruction register	14
7.4 regfile.v — register file with RF_Rp_zero flag.....	15
7.5 alu.v — ALU (reused from earlier lab)	16
7.6 memory.v — unified 256 x 16 memory	16
7.7 program.mem — memory image (annotated summary; the shipped file is 256 bare binary words — see Sec. 10.6).....	18
7.8 risc_core.v — datapath + controller wiring	18
7.9 sevenseg_driver.v — 7-segment scan driver (reused from earlier lab).....	20
7.10 risc_top.v — board top level.....	22
7.11 risc_tb.v — self-checking testbench (simulation only)	24
7.12 nexys_a7_100t.xdc — Nexys A7-100T constraints	26
8. Simulation Results and Waveform Discussion.....	27
8.1 Full-program overview	27

8.2 A closer look: LI → SUB → SW → SRA (180–320 ns).....	28
8.3 Testbench console output	29
9. Board Demonstration	29
10. Problems Encountered and How I Resolved Them.....	31
10.1 The SRA encoding in the handout is inconsistent (found in simulation)	31
10.2 Registered-read memory broke the four-step model (everything off by one)	32
10.3 Blocking assignment in the register file write port.....	32
10.4 Seven-segment ghosting and phantom zeros.....	32
10.5 Divided clock vs. clock enable	33
10.6 \$readmemb file not found — in synthesis but not simulation.....	33
10.7 The dash mode was unobservable — reset scope was too broad	33
11. Conclusion.....	34

2. Problem Statement

The goal of this project is to design, simulate, and implement a small Reduced Instruction Set Computer (RISC) on the Digilent Nexys A7 board (Artix-7 XC7A100T-1CSG324C) using Vivado. The processor executes 16-bit instructions whose leftmost four bits are the opcode, and every functional block in the datapath/controller diagram has to be written as its own Verilog module.

The controller is specified to have exactly two inputs — the 16-bit IR value and a flag RF_Rp_zero from the register file indicating that the value on read port P is zero — and it must sequence every instruction through the same four steps:

1. **Fetch** — read the instruction at memory location PC into the IR,
2. **Decode** — interpret the opcode and register/address fields,
3. **Execute** — perform the operation,
4. **Update PC** — point the PC at the next memory location.

Memory locations 201 and 202 hold initial operand values. The demonstration program below loads them, computes with them, and stores three results at locations 203, 204, and 205, which must appear on the board's 7-segment display once the program has finished:

#	Mnemonic	Encoding
0	LW r5, 201	1001_0101_1100_1001
1	LW r6, 202	1001_0110_1100_1010
2	ADD r7, r5, r6	0000_0111_0101_0110
3	SW r7, 203	1010_0111_1100_1011
4	LI r8, 250	1000_1000_1111_1010
5	SUB r4, r8, r5	0001_0100_1000_0101
6	SW r4, 204	1010_0100_1100_1100
7	SRA r3, r7	0110_0011_0111_0000 *
8	XOR r2, r3, r4	0100_0010_0011_0100
9	SW r2, 205	1010_0010_1100_1101

* The handout gives 0110_0010_0111_0000 for this instruction, whose destination field decodes to r2, not r3. That contradicts both the mnemonic and the following XOR, which reads r3. I use the corrected encoding here; Section 10.1 describes how I found the discrepancy in simulation.

The deliverables are the Verilog modules, a block diagram, ASM-D charts, a controller output table per opcode, simulation results, and this report.

3. Approach

3.1 Multi-cycle organization

I implemented the processor as a multi-cycle machine: one controller FSM state per architectural step, so every instruction takes exactly four states (Fetch, Decode, Execute, UpdatePC). This maps one-to-one onto the four-step process the assignment requires, which makes the controller easy to specify, easy to draw as an ASM-D chart, and easy to check in a waveform — the state register tells you exactly which

step you are looking at. A single-cycle design would have needed separate instruction and data memories (the assignment wants one memory holding both program and data), and a pipelined design is unjustifiable for a ten-instruction demo.

The FSM has a fifth, terminal state, **Halt**. The demo program is ten instructions long and the assignment says results are displayed “once all instructions have executed,” so the machine needs a defined way to stop. I assigned opcode 1111 to a HALT instruction, placed one at address 10 (right after the program), and made the controller park in the Halt state with a done output high. done gates the display and drives LED0, and the testbench uses it to know when to check results.

3.2 One unified memory

Program and data share a single 256×16 -bit memory. Addresses 0–10 hold the program (plus HALT), 201/202 hold the input operands, and 203–205 receive the results. A unified memory means one address bus and a single two-way address mux: during Fetch the address is the PC, and during the Execute step of LW/SW it is the 8-bit address field IR[7:0]. Since the machine is multi-cycle, instruction fetch and data access never happen in the same state, so one port is enough and there is no structural hazard.

The CPU port of the memory uses a **combinational read** with a synchronous write. This is a deliberate choice: with an asynchronous read, the fetched word is available at the memory output in the same state the address is applied, so Fetch and the LW Execute step each fit in a single FSM state and the four-step model stays exact. Vivado infers distributed (LUT) RAM for this style, which costs a few hundred LUTs at 256×16 — cheap on an XC7A100T. My first version used a registered read that maps to block RAM, and the one-cycle read latency quietly broke the four-step model; Section 10.2 covers that bug and why I settled on distributed RAM.

Initial contents (the ten instructions, the HALT, and the operands 25 and 35 at 201/202) are loaded from program.mem with \$readmemb, so the same image feeds both simulation and synthesis.

3.3 Controller

The controller matches the assignment's interface exactly: its only inputs (besides clock, reset, and the clock enable) are IR[15:0] and RF_Rp_zero. It is a five-state FSM (the four steps plus Halt). All outputs are generated in a single combinational block with default assignments first, so no latches are inferred; the opcode IR[15:12] selects the Execute-step outputs, and RF_Rp_zero is consulted in exactly one place.

About that flag: none of the ten demo instructions is conditional, but the assignment specifies RF_Rp_zero as a controller input, so I gave it a real job rather than leaving a dangling port. I defined a conditional branch, JZ rs, addr (opcode 1100, same field layout as SW): if the register on read port P is zero, the PC loads IR[7:0] in the UpdatePC step instead of incrementing. The demo program never executes a JZ, but the path is implemented, simulated, and documented in the controller table, and it is the reason the PC has a load input as well as an increment.

3.4 Reuse of previously developed modules

Two blocks in this design are adaptations of modules I built earlier in the course rather than new work:

- **ALU/shifter** (alu.v): the arithmetic unit from the earlier combinational-design lab, trimmed to the four operations this ISA needs (ADD, SUB, XOR, and a one-bit arithmetic right shift). The shift is the sign-replicating {a[15], a[15:1]} slice from the lab shifter; I removed the ops this project doesn't use rather than carrying dead logic through synthesis.
- **7-segment scan driver** (sevensseg_driver.v): the multiplexed 8-digit driver from the display lab. For this project I added a per-digit blanking mask (to insert dark separator digits between the three result bytes) and a “dash mode” that shows -- -- while the CPU is still running, so the display state distinguishes “running” from “done” at a glance.

Everything else — PC, IR, register file, memory, controller, and the top level — was written new for this project, one module per box in the block diagram.

3.5 Register file and instruction formats

The register file is 16×16 -bit with two combinational read ports (P and Q) and one synchronous write port. Port P also produces the RF_Rp_zero flag (rp_data == 0) required by the controller. The instruction formats decode as:

Format	Opcode(s)	Bits [15:12]	Bits [11:8]	Bits [7:0]
R-type	ADD 0000, SUB 0001, XOR 0100	opcode	rd	rs [7:4], rt [3:0]
Shift	SRA 0110	opcode	rd	rs [7:4], unused [3:0]
LI	1000	opcode	rd	imm8 (zero-extended)
LW	1001	opcode	rd	addr8
SW	1010	opcode	rs	addr8
JZ	1100	opcode	rs	addr8
HALT	1111	opcode	unused	unused

One decode wrinkle: for SW and JZ the source register sits in bits [11:8], where every other format keeps the destination. Rather than add a third read port, read port P's address comes through a small mux (rf_rp_addr_sel): normally IR[7:4] (rs), but IR[11:8] during the Execute step of SW/JZ. The store data path is then simply port P into the memory's write-data input.

LI zero-extends its 8-bit immediate; with values up to 250 in the demo program, sign extension would corrupt anything above 127. SRA shifts by one bit with sign replication, which matches the expected result (SRA of 60 $\rightarrow$ 30).

3.6 Initial data and hand-calculated results

I chose mem[201] = 25 and mem[202] = 35. Every intermediate value is distinct and each instruction visibly changes state, so a single waveform pass verifies all of them:

#	Instruction	Effect	Value
0	LW r5, 201	r5 $\leftarrow$ mem[201]	25
1	LW r6, 202	r6 $\leftarrow$ mem[202]	35
2	ADD r7, r5, r6	r7 $\leftarrow$ 25 + 35	60

3	SW r7, 203	mem[203] ← r7	60 (0x3C)
4	LI r8, 250	r8 ← 250	250
5	SUB r4, r8, r5	r4 ← 250 – 25	225
6	SW r4, 204	mem[204] ← r4	225 (0xE1)
7	SRA r3, r7	r3 ← 60 >>> 1	30
8	XOR r2, r3, r4	r2 ← 0x001E ^ 0x00E1	255
9	SW r2, 205	mem[205] ← r2	255 (0xFF)

The XOR is worth spelling out: 30 = 0001_1110, 225 = 1110_0001; the operands are bitwise complements over the low byte, so the result is 1111_1111 = 255. The display therefore ends at 3C E1 FF.

3.7 Clocking, reset, and the display path


The whole design runs in a single 100 MHz clock domain. The CPU is throttled by a **clock enable** — a one-cycle pulse every 100 clocks (1 MHz architectural rate) — rather than a divided clock. Every sequential element in the core (PC, IR, register file write, memory write, FSM state) qualifies its update with en, while the display logic runs at the full 100 MHz. My first attempt used a divided clock and turned into a two-clock-domain design with CDC warnings; Section 10.5 explains the switch. At 1 MHz the program finishes in about 44 μs — instant to the eye, but the rate is trivially adjustable if I ever want to single-step with a slower enable.


Reset is the center pushbutton (BTNC), taken through a two-flop synchronizer. Because it is a level reset and the FSM only advances once every 100 clocks, contact bounce just stretches the reset interval; no separate debouncer is needed.

For output, the memory has a second, read-only combinational port that the CPU never uses. A small scanner in the top level continuously cycles it through addresses 203/204/205 and latches the three words into result registers. The display shows the low byte of each in hex across the eight digits as 3C E1 FF (digit pairs 7–6, 4–3, 1–0, with digits 5 and 2 blanked as separators). Until done goes high the enabled digits show dashes, so the board visibly distinguishes reset/running from finished. I chose hex over decimal because three 3-digit decimal numbers need nine digits — one more than the board has — while hex is unambiguous, and the report and testbench give the decimal equivalents.

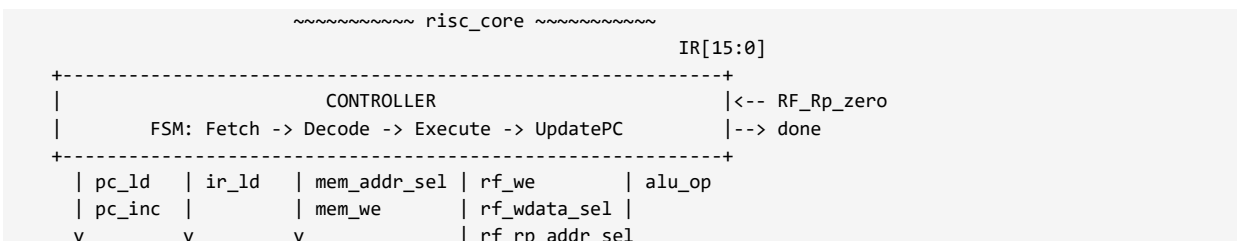4. Block Diagram


Every box below is one Verilog module (one file each); `risc_core.v` instantiates the six core blocks plus the three datapath muxes, and `risc_top.v` adds the board-level blocks. (I redraw this figure by hand for the submitted diagram; the ASCII version is the authoritative wiring reference.)



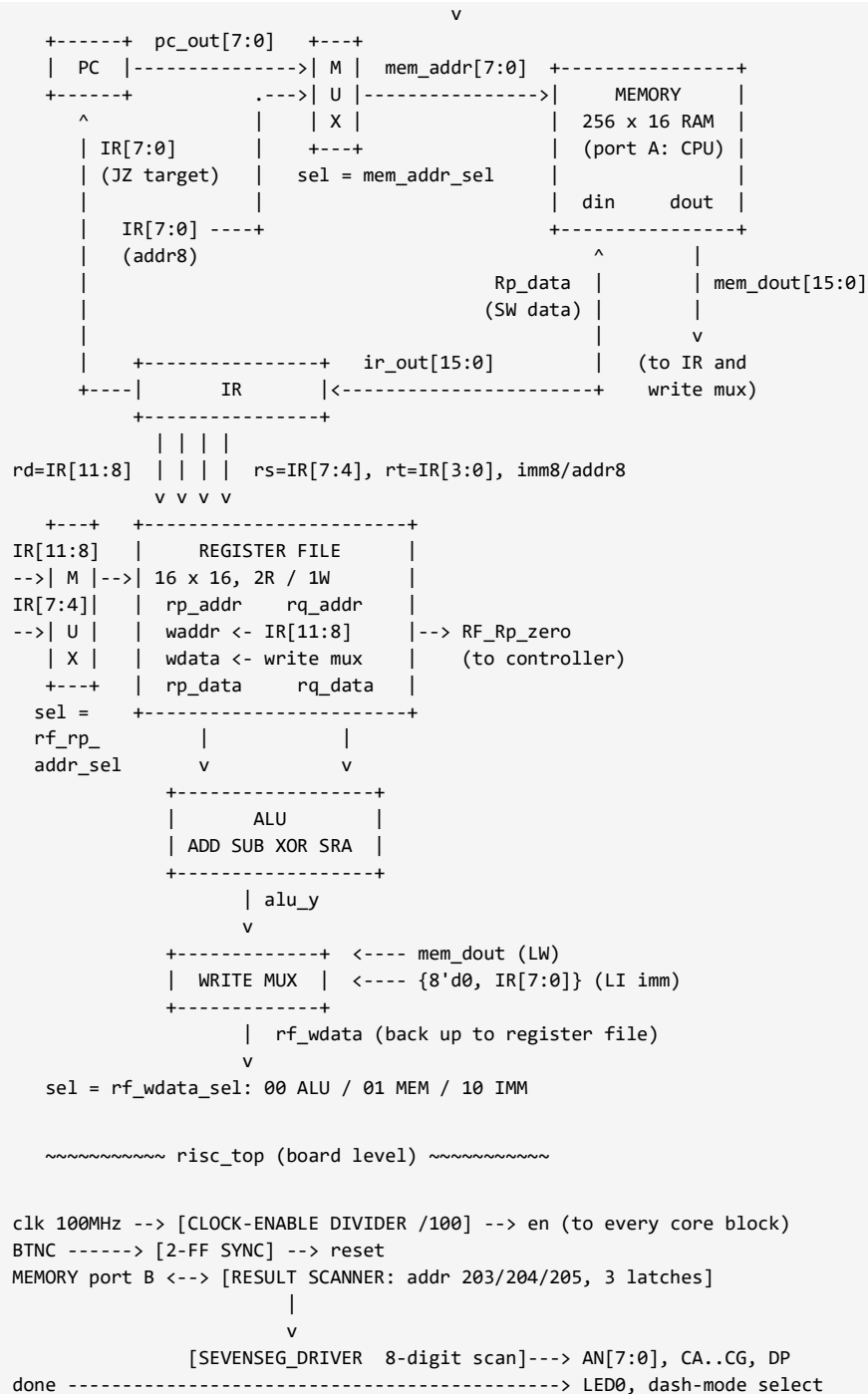


Drawing conventions: rectangles are states (Moore outputs listed beside them), angle-bracket diamonds are decisions, and rounded (parenthesized) boxes are conditional outputs valid within the state they

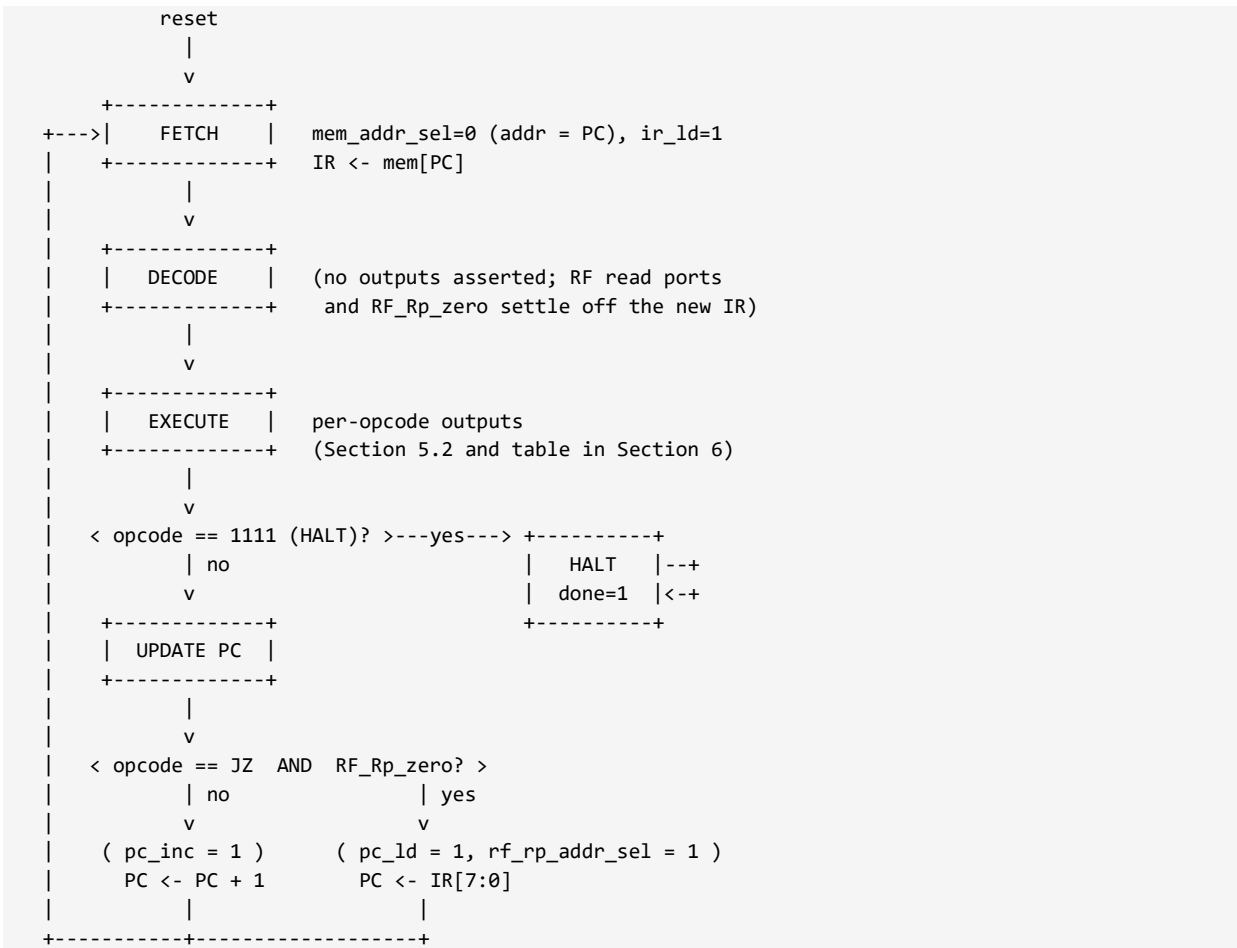hang off. Every register transfer written next to a state happens on the clock-enable edge that leaves that state.



In words: out of reset the FSM sits in FETCH with the address mux pointed at the PC and `ir_ld` asserted, so the instruction word is captured into the IR on the state-exit edge. DECODE asserts nothing; it exists so the register file's combinational read ports (and the `RF_Rp_zero` flag) settle a full state before EXECUTE uses them, and it is where the opcode fields become valid to the controller. EXECUTE raises the per-opcode signals from the Section 6 table. The HALT test hangs off EXECUTE: opcode 1111 sends the machine to the terminal HALT state, which holds `done` high forever (only reset leaves it). UPDATE PC is the one place `RF_Rp_zero` matters — a JZ whose source register read zero loads the branch target `IR[7:0]` into the PC; every other case increments.

5.2 Execute-step branching per opcode

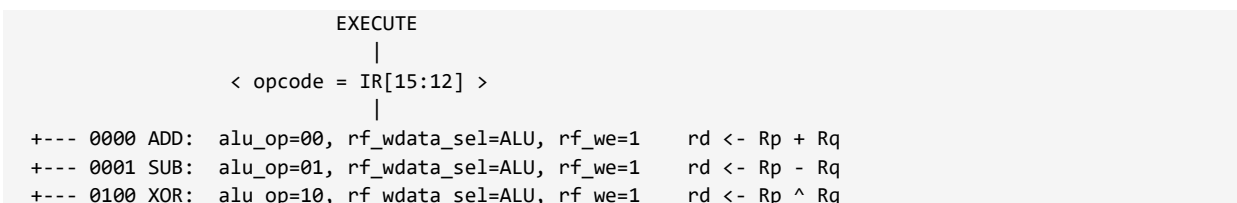

```

+--- 0110 SRA: alu_op=11, rf_wdata_sel=ALU, rf_we=1    rd <- {Rp[15],Rp[15:1]}
+--- 1000 LI : rf_wdata_sel=IMM, rf_we=1              rd <- {8'd0, IR[7:0]}
+--- 1001 LW : mem_addr_sel=1, rf_wdata_sel=MEM,      rd <- mem[IR[7:0]]
|              rf_we=1
+--- 1010 SW : mem_addr_sel=1, rf_rp_addr_sel=1,      mem[IR[7:0]] <- Rp
|              mem_we=1                             (Rp = r[IR[11:8]])
+--- 1100 JZ : rf_rp_addr_sel=1                      (branch resolves in
|                                                    UPDATE PC)
+--- 1111 HALT: (no outputs; next state = HALT)

```

6. Controller Output Table

Signals: PC_ld, PC_inc (program counter), IR_ld (instruction register), MemSel = mem_addr_sel (0 = PC, 1 = IR[7:0]), Mem_we, RF_we, WSel = rf_wdata_sel (00 = ALU, 01 = memory, 10 = immediate), RpSel = rf_rp_addr_sel (0 = IR[7:4], 1 = IR[11:8]), ALU = alu_op (00 ADD, 01 SUB, 10 XOR, 11 SRA), done. Unlisted values are 0; “—” means don't-care (the default 0/00 is emitted so the logic stays latch-free).

Steps common to every opcode:

Step	PC_ld	PC_inc	IR_ld	MemSel	Mem_we	RF_we	WSel	RpSel	ALU	done
Fetch	0	0	1	0	0	0	—	—	—	0
Decode	0	0	0	—	0	0	—	—	—	0
UpdatePC (all but taken JZ)	0	1	0	—	0	0	—	—	—	0
UpdatePC (JZ, RF_Rp_zero=1)	1	0	0	—	0	0	—	1	—	0
Halt (terminal state)	0	0	0	—	0	0	—	—	—	1

Execute step, by opcode:

Opcode	Instr	PC_ld	PC_inc	IR_ld	MemSel	Mem_we	RF_we	WSel	RpSel	ALU	done
0000	ADD	0	0	0	—	0	1	00	0	00	0
0001	SUB	0	0	0	—	0	1	00	0	01	0
0100	XOR	0	0	0	—	0	1	00	0	10	0
0110	SRA	0	0	0	—	0	1	00	0	11	0
1000	LI	0	0	0	—	0	1	10	—	—	0
1001	LW	0	0	0	1	0	1	01	—	—	0
1010	SW	0	0	0	1	1	0	—	1	—	0
1100	JZ	0	0	0	—	0	0	—	1	—	0
1111	HALT	0	0	0	—	0	0	—	—	—	0

Notes: SW and JZ set RpSel = 1 because their source register is in IR[11:8]. JZ asserts nothing else in Execute — it only steers read port P so that RF_Rp_zero reflects the tested register; the actual PC action happens in UpdatePC. HALT's Execute step is a no-op whose only effect is the transition into the terminal Halt state.

7. Verilog Code

All modules are Verilog-2001, one file per block, written to synthesize cleanly in Vivado (no latches, single clock domain, memory styles chosen to infer distributed RAM). The testbench is simulation-only.

7.1 controller.v — the FSM controller

```
`timescale 1ns / 1ps
//-----
// controller.v -- four-state FSM controller (Fetch / Decode / Execute / UpdatePC)
// EE 5193 FPGA and HDL, Summer 2026 -- RISC project
// Sergio Arreola
//
// Inputs, exactly as the assignment specifies: the 16-bit IR value and the
// RF_Rp_zero flag from the register file. The FSM walks the four required
// steps for every instruction and branches on the opcode (IR[15:12]) only
// inside the Execute and UpdatePC steps. RF_Rp_zero is consulted only by
// the conditional branch JZ; a HALT opcode parks the machine in a fifth,
// terminal state and raises `done` for the testbench and the display.
//
// State register updates are qualified by `en` (the CPU clock enable), so
// each architectural step lasts one enable period. Outputs are a pure
// function of (state, opcode, rp_zero) -- Moore-style states with a Mealy
// branch decision in UpdatePC -- generated in one combinational block with
// default assignments first, so no latches are inferred.
//-----
module controller (
    input wire      clk,
    input wire      reset,          // synchronous, active high
    input wire      en,             // CPU clock enable
    input wire [15:0] ir,           // instruction register value
    input wire      rf_rp_zero,     // register file read-port-P == 0 flag

    // PC controls
    output reg      pc_ld,          // load branch target (taken JZ)
    output reg      pc_inc,         // PC <- PC + 1
    // IR control
    output reg      ir_ld,          // capture memory output into IR
    // Memory controls
    output reg      mem_addr_sel,   // 0: addr = PC (fetch), 1: addr = IR[7:0]
    output reg      mem_we,        // memory write (SW)
    // Register file controls
    output reg      rf_we,          // register write (ADD/SUB/XOR/SRA/LI/LW)
    output reg [1:0] rf_wdata_sel, // 00: ALU, 01: memory, 10: zero-ext imm8
    output reg      rf_rp_addr_sel, // 0: Rp addr = IR[7:4], 1: IR[11:8] (SW/JZ)
    // ALU control
    output reg [1:0] alu_op,        // 00 ADD, 01 SUB, 10 XOR, 11 SRA
    // Status
    output reg      done            // program finished (HALT reached)
);

// Opcodes (IR[15:12])
localparam [3:0] OP_ADD  = 4'b0000,
                OP_SUB  = 4'b0001,
                OP_XOR  = 4'b0100,
                OP_SRA  = 4'b0110,
                OP_LI   = 4'b1000,
                OP_LW   = 4'b1001,
                OP_SW   = 4'b1010,
                OP_JZ   = 4'b1100, // branch if Rp == 0 (uses RF_Rp_zero)
                OP_HALT = 4'b1111;

// Write-data mux encodings
localparam [1:0] WD_ALU = 2'b00,
                WD_MEM  = 2'b01,
                WD_IMM  = 2'b10;
```

```

// States: the four required steps plus a terminal halt state
localparam [2:0] S_FETCH  = 3'd0,
                S_DECODE = 3'd1,
                S_EXEC    = 3'd2,
                S_UPDATE  = 3'd3,
                S_HALT    = 3'd4;

reg [2:0] state, next_state;

wire [3:0] opcode = ir[15:12];

// ---- state register -----
always @(posedge clk) begin
    if (reset)
        state <= S_FETCH;
    else if (en)
        state <= next_state;
end

// ---- next-state logic -----
always @* begin
    case (state)
        S_FETCH: next_state = S_DECODE;
        S_DECODE: next_state = S_EXEC;
        S_EXEC:   next_state = (opcode == OP_HALT) ? S_HALT : S_UPDATE;
        S_UPDATE: next_state = S_FETCH;
        S_HALT:   next_state = S_HALT;
        default:  next_state = S_FETCH;
    endcase
end

// ---- output logic -----
// Defaults first so every path is covered and nothing infers a latch.
always @* begin
    pc_ld      = 1'b0;
    pc_inc     = 1'b0;
    ir_ld      = 1'b0;
    mem_addr_sel = 1'b0;    // default: address = PC
    mem_we     = 1'b0;
    rf_we      = 1'b0;
    rf_wdata_sel = WD_ALU;
    rf_rp_addr_sel = 1'b0;  // default: Rp reads rs = IR[7:4]
    alu_op      = 2'b00;
    done        = 1'b0;

    case (state)
        // Step 1: instruction at mem[PC] into IR
        S_FETCH: begin
            mem_addr_sel = 1'b0;
            ir_ld        = 1'b1;
        end

        // Step 2: opcode/fields settle; register file read ports and
        // the RF_Rp_zero flag become valid. No register is written.
        S_DECODE: begin
            // no asserted outputs -- decode is combinational off the IR
        end
    endcase
end

```

```

// Step 3: per-opcode work
S_EXEC: begin
  case (opcode)
    OP_ADD: begin
      alu_op      = 2'b00;
      rf_wdata_sel = WD_ALU;
      rf_we        = 1'b1;
    end
    OP_SUB: begin
      alu_op      = 2'b01;
      rf_wdata_sel = WD_ALU;
      rf_we        = 1'b1;
    end
    OP_XOR: begin
      alu_op      = 2'b10;
      rf_wdata_sel = WD_ALU;
      rf_we        = 1'b1;
    end
    OP_SRA: begin
      alu_op      = 2'b11;
      rf_wdata_sel = WD_ALU;
      rf_we        = 1'b1;
    end
    OP_LI: begin
      rf_wdata_sel = WD_IMM;
      rf_we        = 1'b1;
    end
    OP_LW: begin
      mem_addr_sel = 1'b1;    // address = IR[7:0]
      rf_wdata_sel = WD_MEM;
      rf_we        = 1'b1;
    end
    OP_SW: begin
      mem_addr_sel = 1'b1;    // address = IR[7:0]
      rf_rp_addr_sel = 1'b1;  // Rp reads rs = IR[11:8]
      mem_we        = 1'b1;
    end
    OP_JZ: begin
      rf_rp_addr_sel = 1'b1;  // Rp reads rs = IR[11:8];
                                // branch resolves in UpdatePC
    end
    default: ;                // OP_HALT and unused opcodes
  endcase
end

// Step 4: next sequential address, or the branch target for a
// taken JZ (this is the one place RF_Rp_zero is used)
S_UPDATE: begin
  if (opcode == OP_JZ && rf_rp_zero) begin
    rf_rp_addr_sel = 1'b1;    // keep rs selected so the
    pc_ld          = 1'b1;    // flag stays valid
  end else begin
    pc_inc = 1'b1;
  end
end

S_HALT: begin
  done = 1'b1;
end

default: ;
endcase

```

```

end

endmodule

```

7.2 pc.v — program counter

```

`timescale 1ns / 1ps
//-----
// pc.v -- 8-bit program counter
// EE 5193 FPGA and HDL, Summer 2026 -- RISC project
// Sergio Arreola
//
// Holds the address of the current instruction. Supports synchronous load
// (for taken branches) and increment (UpdatePC step). Load has priority over
// increment; the controller never asserts both. All updates are qualified by
// the CPU clock enable `en` so the whole core can be throttled from the
// 100 MHz board clock without a derived clock.
//-----
module pc (
    input wire      clk,
    input wire      reset, // synchronous, active high
    input wire      en,    // CPU clock enable
    input wire      ld,    // load pc_in (branch target)
    input wire      inc,    // pc <= pc + 1
    input wire [7:0] pc_in, // branch target from IR[7:0]
    output reg [7:0] pc_out
);

    always @(posedge clk) begin
        if (reset)
            pc_out <= 8'd0;
        else if (en) begin
            if (ld)
                pc_out <= pc_in;
            else if (inc)
                pc_out <= pc_out + 8'd1;
        end
    end

endmodule

```

7.3 ir.v — instruction register

```

`timescale 1ns / 1ps
//-----
// ir.v -- 16-bit instruction register
// EE 5193 FPGA and HDL, Summer 2026 -- RISC project
// Sergio Arreola
//
// Captures the memory output word at the end of the Fetch step. The
// controller decodes ir_out directly; the fields are
//   ir_out[15:12] opcode
//   ir_out[11:8]  rd (or rs for SW/JZ)
//   ir_out[7:4]   rs
//   ir_out[3:0]   rt

```

```
// ir_out[7:0]  imm8 / addr8
//-----
module ir (
    input wire      clk,
    input wire      reset,    // synchronous, active high
    input wire      en,       // CPU clock enable
    input wire      ld,       // capture ir_in
    input wire [15:0] ir_in,   // memory read data
    output reg [15:0] ir_out
);

    always @(posedge clk) begin
        if (reset)
            ir_out <= 16'd0;
        else if (en && ld)
            ir_out <= ir_in;
        end

endmodule
```

7.4 regfile.v — register file with RF_Rp_zero flag

```
`timescale 1ns / 1ps
//-----
// regfile.v -- 16 x 16-bit register file, 2 read ports / 1 write port
// EE 5193 FPGA and HDL, Summer 2026 -- RISC project
// Sergio Arreola
//
// Read ports are combinational (the Decode step gives the read data a full
// state period to settle before the Execute step uses it). The write port is
// synchronous and qualified by the CPU clock enable. Writes use a
// non-blocking assignment so a read and a write in the same cycle return the
// OLD register value -- see the report, "Problems encountered", for the
// blocking-assignment bug this replaced.
//
// rp_zero is the flag required by the assignment: it is high whenever the
// value currently presented on read port P is zero. The controller samples
// it during Execute to resolve the conditional branch (JZ).
//-----
module regfile (
    input wire      clk,
    input wire      en,       // CPU clock enable
    input wire      we,       // write enable (Execute step of writing ops)
    input wire [3:0] waddr,    // destination register rd
    input wire [15:0] wdata,    // from write-data mux (ALU / mem / imm)
    input wire [3:0] rp_addr,  // read port P address
    input wire [3:0] rq_addr,  // read port Q address
    output wire [15:0] rp_data,
    output wire [15:0] rq_data,
    output wire      rp_zero   // flag to controller: rp_data == 0
);

    reg [15:0] rf [0:15];

    integer i;
    initial begin
        for (i = 0; i < 16; i = i + 1)
            rf[i] = 16'd0;
    end
```

```

end

always @(posedge clk) begin
    if (en && we)
        rf[waddr] <= wdata;
    end

    assign rp_data = rf[rp_addr];
    assign rq_data = rf[rq_addr];
    assign rp_zero = (rp_data == 16'd0);

endmodule

```

7.5 alu.v — ALU (reused from earlier lab)

```

`timescale 1ns / 1ps
//-----
// alu.v -- 16-bit ALU: ADD, SUB, XOR, SRA
// EE 5193 FPGA and HDL, Summer 2026 -- RISC project
// Sergio Arreola
//
// Adapted from the ALU/shifter developed in the earlier combinational-logic
// lab; trimmed to the four operations this instruction set needs. Purely
// combinational. SRA shifts operand A right by one with sign replication
// (operand B is ignored for that op).
//-----
module alu (
    input wire [15:0] a,      // register file read port P
    input wire [15:0] b,      // register file read port Q
    input wire [1:0] op,      // 00 ADD, 01 SUB, 10 XOR, 11 SRA
    output reg [15:0] y
);

    localparam [1:0] ALU_ADD = 2'b00,
                     ALU_SUB = 2'b01,
                     ALU_XOR = 2'b10,
                     ALU_SRA = 2'b11;

    always @* begin
        case (op)
            ALU_ADD: y = a + b;
            ALU_SUB: y = a - b;
            ALU_XOR: y = a ^ b;
            ALU_SRA: y = {a[15], a[15:1]}; // arithmetic shift right by 1
            default: y = 16'd0;
        endcase
    end

endmodule

```

7.6 memory.v — unified 256 x 16 memory

```

`timescale 1ns / 1ps
//-----

```



```

// memory.v -- unified 256 x 16-bit instruction/data memory
// EE 5193 FPGA and HDL, Summer 2026 -- RISC project
// Sergio Arreola
//
// One memory holds both the program (addresses 0..10) and the data
// (201/202 in, 203..205 out), so a single address mux switches the CPU
// between fetching (addr = PC) and load/store (addr = IR[7:0]).
//
// Port A is the CPU port: combinational read, synchronous write. The
// combinational read is deliberate -- it lets Fetch and LW each complete in
// one FSM state. Vivado infers distributed (LUT) RAM for this, which is
// cheap at 256x16. I originally wrote a registered-read version that maps
// to block RAM, but the one-cycle read latency broke the four-state execute
// model (see "Problems encountered" in the report).
//
// Port B is a read-only combinational port used only by the display logic
// in the top level to scan mem[203..205]; the CPU never touches it.
//
// Initial contents come from program.mem via $readmemb: the ten demo
// instructions plus a HALT at 0..10, the operands 25/35 at 201/202, and
// zeros everywhere else. The file lists all 256 words in order with no
// @ address jumps and no comments -- Vivado synthesis's $readmemb parser
// rejects both (it reads @ addresses as binary, unlike xsim, which
// follows the LRM and reads them as hex). See "Problems encountered".
//-----
module memory #(
    parameter MEM_INIT_FILE = "program.mem"
) (
    input wire      clk,
    input wire      en,          // CPU clock enable
    input wire      we,          // write enable (Execute step of SW)
    input wire [7:0] addr,       // port A address (PC or IR[7:0])
    input wire [15:0] din,       // store data (register file port P)
    output wire [15:0] dout,     // port A read data
    input wire [7:0] addr_b,     // port B address (display scan)
    output wire [15:0] dout_b    // port B read data
);

    reg [15:0] ram [0:255];

    initial begin
        $readmemb(MEM_INIT_FILE, ram);    // file covers all 256 addresses
    end

    always @(posedge clk) begin
        if (en && we)
            ram[addr] <= din;
    end

    assign dout  = ram[addr];
    assign dout_b = ram[addr_b];

endmodule

```

7.7 program.mem — memory image (annotated summary; the shipped file is 256 bare binary words — see Sec. 10.6)

Annotated contents of src/program.mem

=====

The shipped file is 256 bare 16-bit binary words, one per line, where line N holds memory address N-1. No comments and no @ address jumps -- Vivado synthesis's \$readmemb parser rejects both (see report Sec. 10.6). All words not listed below are 0000000000000000.

addr	word	official meaning
0	1001010111001001	LW r5, 201 r5 <- mem[201] = 25
1	1001011011001010	LW r6, 202 r6 <- mem[202] = 35
2	0000011010101110	ADD r7, r5, r6 r7 <- 25 + 35 = 60
3	1010011111001011	SW r7, 203 mem[203] <- 60
4	1000100011111010	LI r8, 250 r8 <- 250
5	0001010010000101	SUB r4, r8, r5 r4 <- 250 - 25 = 225
6	1010010011001100	SW r4, 204 mem[204] <- 225
7	0110001101110000	SRA r3, r7 r3 <- 60 >>> 1 = 30 (rd field corrected from the handout's 0010; see report Sec. 10.1)
8	0100001000110100	XOR r2, r3, r4 r2 <- 30 ^ 225 = 255
9	1010001011001101	SW r2, 205 mem[205] <- 255
10	1111000000000000	HALT
201	00000000000011001	25 (input operand)
202	0000000000100011	35 (input operand)

7.8 risc_core.v — datapath + controller wiring

```
`timescale 1ns / 1ps
//-----
// risc_core.v -- datapath + controller wired together (board-independent)
// EE 5193 FPGA and HDL, Summer 2026 -- RISC project
// Sergio Arreola
//
// Every box in the block diagram is its own module instance; this file is
// only wiring plus the three datapath muxes (memory address, register file
// write data, register file Rp read address). Keeping the core free of any
// board logic lets the same module sit under both the testbench (en tied
// high) and risc_top (en driven by the clock-enable divider).
//-----
module risc_core #(
    parameter MEM_INIT_FILE = "program.mem"
) (
    input wire      clk,
    input wire      reset,      // synchronous, active high
    input wire      en,         // CPU clock enable
    output wire     done,       // HALT reached
    // display-side memory read port (used by risc_top, idle in simulation)
    input wire [7:0] disp_addr,
    output wire [15:0] disp_data
);

// ---- interconnect -----
wire [7:0] pc_out;
wire [15:0] ir_out;
wire [15:0] mem_dout;
```

```

wire [15:0] rf_rp_data, rf_rq_data;
wire [15:0] alu_y;
wire        rf_rp_zero;

// control signals
wire        pc_ld, pc_inc, ir_ld;
wire        mem_addr_sel, mem_we;
wire        rf_we, rf_rp_addr_sel;
wire [1:0]  rf_wdata_sel;
wire [1:0]  alu_op;

// ---- datapath muxes -----
// memory address: PC during Fetch, IR[7:0] during LW/SW Execute
wire [7:0] mem_addr = mem_addr_sel ? ir_out[7:0] : pc_out;

// register file read port P address: rs field, except SW/JZ where the
// source register lives in bits [11:8]
wire [3:0] rp_addr = rf_rp_addr_sel ? ir_out[11:8] : ir_out[7:4];

// register file write data: ALU result / memory word / zero-extended imm8
reg [15:0] rf_wdata;
always @* begin
    case (rf_wdata_sel)
        2'b01: rf_wdata = mem_dout;           // LW
        2'b10: rf_wdata = {8'd0, ir_out[7:0]}; // LI
        default: rf_wdata = alu_y;           // ADD/SUB/XOR/SRA
    endcase
end

// ---- module instances -----
controller u_ctrl (
    .clk          (clk),
    .reset        (reset),
    .en           (en),
    .ir           (ir_out),
    .rf_rp_zero   (rf_rp_zero),
    .pc_ld        (pc_ld),
    .pc_inc       (pc_inc),
    .ir_ld        (ir_ld),
    .mem_addr_sel (mem_addr_sel),
    .mem_we       (mem_we),
    .rf_we        (rf_we),
    .rf_wdata_sel (rf_wdata_sel),
    .rf_rp_addr_sel (rf_rp_addr_sel),
    .alu_op       (alu_op),
    .done         (done)
);

pc u_pc (
    .clk   (clk),
    .reset (reset),
    .en    (en),
    .ld    (pc_ld),
    .inc    (pc_inc),
    .pc_in (ir_out[7:0]), // JZ branch target
    .pc_out (pc_out)
);

ir u_ir (
    .clk   (clk),

```

```

        .reset (reset),
        .en    (en),
        .ld    (ir_ld),
        .ir_in (mem_dout),
        .ir_out (ir_out)
    );

    regfile u_rf (
        .clk    (clk),
        .en      (en),
        .we      (rf_we),
        .waddr   (ir_out[11:8]), // rd
        .wdata   (rf_wdata),
        .rp_addr (rp_addr),
        .rq_addr (ir_out[3:0]),  // rt
        .rp_data (rf_rp_data),
        .rq_data (rf_rq_data),
        .rp_zero (rf_rp_zero)
    );

    alu u_alu (
        .a (rf_rp_data),
        .b (rf_rq_data),
        .op (alu_op),
        .y (alu_y)
    );

    memory #(.MEM_INIT_FILE(MEM_INIT_FILE)) u_mem (
        .clk    (clk),
        .en      (en),
        .we      (mem_we),
        .addr    (mem_addr),
        .din     (rf_rp_data), // SW store data
        .dout    (mem_dout),
        .addr_b  (disp_addr),
        .dout_b  (disp_data)
    );

endmodule

```

7.9 sevenseg_driver.v — 7-segment scan driver (reused from earlier lab)

```

`timescale 1ns / 1ps
//-----
// sevenseg_driver.v -- 8-digit multiplexed 7-segment scan driver (Nexys A7)
// EE 5193 FPGA and HDL, Summer 2026 -- RISC project
// Sergio Arreola
//
// Reused from my earlier display lab, with two additions for this project:
// a per-digit blanking mask (digit_en) and a dash mode used while the CPU
// is still running. Anodes and cathodes are both active low on the Nexys A7.
//
// The driver deliberately has NO reset: its outputs are a pure function of
// the free-running scan counter and the current inputs, so the display keeps
// scanning -- showing dashes -- while the CPU is held in reset by BTNC. My
// first version reset the driver along with the CPU, which blanked the whole
// display during reset and made the dash mode unobservable (see "Problems
// encountered"). Registers carry initial values for simulation; on the FPGA

```

```

// the GSR provides the same power-up state.
//
// Scan rate: the digit select comes from bits [19:17] of a free-running
// counter at 100 MHz, so each digit is lit for  $2^{17} * 10 \text{ ns} = 1.31 \text{ ms}$  and
// the full 8-digit frame refreshes at ~95 Hz -- fast enough not to flicker,
// slow enough that the anode drivers settle (see "Problems encountered"
// for the ghosting I got with a faster scan and no blanking).
//
// seg bit order: seg[6:0] = {CG,CF,CE,CD,CC,CB,CA}, i.e. seg[0] = CA.
//-----
module sevenseg_driver (
    input wire      clk,          // 100 MHz board clock
    input wire [31:0] digits,     // 8 hex nibbles, digit 7 = digits[31:28]
    input wire [7:0] digit_en,    // 1 = display this digit, 0 = blank
    input wire      show_dash,    // 1 = enabled digits show '-'
    output reg [7:0] an,          // anodes, active low
    output reg [6:0] seg,         // cathodes CG..CA, active low
    output wire     dp           // decimal point, active low (kept off)
);

    assign dp = 1'b1;            // decimal point never used

    // ---- scan counter (free-running, never reset) -----
    reg [19:0] scan_cnt = 20'd0;
    always @(posedge clk)
        scan_cnt <= scan_cnt + 20'd1;

    wire [2:0] digit_sel = scan_cnt[19:17];

    // ---- current nibble -----
    reg [3:0] nibble;
    always @* begin
        case (digit_sel)
            3'd0: nibble = digits[3:0];
            3'd1: nibble = digits[7:4];
            3'd2: nibble = digits[11:8];
            3'd3: nibble = digits[15:12];
            3'd4: nibble = digits[19:16];
            3'd5: nibble = digits[23:20];
            3'd6: nibble = digits[27:24];
            3'd7: nibble = digits[31:28];
        endcase
    end

    // ---- hex-to-segment decode (active low, {g,f,e,d,c,b,a}) -----
    reg [6:0] hex_seg;
    always @* begin
        case (nibble)
            4'h0: hex_seg = 7'b1000000;
            4'h1: hex_seg = 7'b1111001;
            4'h2: hex_seg = 7'b0100100;
            4'h3: hex_seg = 7'b0110000;
            4'h4: hex_seg = 7'b0011001;
            4'h5: hex_seg = 7'b0010010;
            4'h6: hex_seg = 7'b0000010;
            4'h7: hex_seg = 7'b1111000;
            4'h8: hex_seg = 7'b0000000;
            4'h9: hex_seg = 7'b0010000;
            4'hA: hex_seg = 7'b0001000;
            4'hB: hex_seg = 7'b0000011;
            4'hC: hex_seg = 7'b1000110;
        endcase
    end

```

```

        4'hD: hex_seg = 7'b0100001;
        4'hE: hex_seg = 7'b0000110;
        4'hF: hex_seg = 7'b0001110;
    endcase
end

localparam [6:0] SEG_DASH = 7'b0111111; // segment G only
localparam [6:0] SEG_BLANK = 7'b1111111;

// ---- registered outputs (anode and cathode switch together) -----
initial begin
    an = 8'hFF;
    seg = SEG_BLANK;
end

always @(posedge clk) begin
    if (digit_en[digit_sel]) begin
        an <= ~(8'd1 << digit_sel);
        seg <= show_dash ? SEG_DASH : hex_seg;
    end else begin
        an <= 8'hFF; // blank digit: no anode driven
        seg <= SEG_BLANK;
    end
end

endmodule

```

7.10 risc_top.v — board top level

```

`timescale 1ns / 1ps
//-----
// risc_top.v -- board top level for the Nexys A7-100T
// EE 5193 FPGA and HDL, Summer 2026 -- RISC project
// Sergio Arreola
//
// Wires the CPU core to the board: 100 MHz clock in, BTNC as reset,
// mem[203]/mem[204]/mem[205] out on the 7-segment display in hex as
//      [203] _ [204] _ [205]  ->  "3C E1 FF"
// (digits 7-6, 4-3, 1-0; digits 5 and 2 blanked as separators). While the
// program is still running the display shows dashes; LED0 lights when the
// HALT instruction is reached.
//
// Clocking: everything runs on the raw 100 MHz clock. The CPU is throttled
// with a clock ENABLE that pulses once per 100 cycles (1 MHz architectural
// rate) instead of a divided clock -- my first attempt used a divided clock
// as a second clock domain and produced CDC warnings and a failing timing
// setup; the clock-enable version keeps one clean clock domain (see
// "Problems encountered").
//-----
module risc_top (
    input wire      clk,        // 100 MHz board clock (E3)
    input wire      btnC,       // center pushbutton = reset, active high
    output wire [7:0] an,        // 7-seg anodes, active low
    output wire [6:0] seg,       // 7-seg cathodes CG..CA, active low
    output wire      dp,         // decimal point, active low
    output wire      led0        // done indicator
);

```

```

// ---- reset synchronizer -----
// BTNC is asynchronous; two flops synchronize it into the clock domain.
// The FSM only samples state changes every 100 clocks (cpu_en), so any
// residual contact bounce (~ms) just holds reset a little longer --
// no separate debouncer is needed for a level-sensitive reset.
reg [1:0] rst_sync;
always @(posedge clk)
    rst_sync <= {rst_sync[0], btnC};
wire reset = rst_sync[1];

// ---- CPU clock enable: 1 pulse every 100 clocks (1 MHz) -----
reg [6:0] ce_cnt;
reg      cpu_en;
always @(posedge clk) begin
    if (reset) begin
        ce_cnt <= 7'd0;
        cpu_en <= 1'b0;
    end else if (ce_cnt == 7'd99) begin
        ce_cnt <= 7'd0;
        cpu_en <= 1'b1;
    end else begin
        ce_cnt <= ce_cnt + 7'd1;
        cpu_en <= 1'b0;
    end
end

// ---- CPU core -----
wire      done;
wire [7:0] disp_addr;
wire [15:0] disp_data;

risc_core #(.MEM_INIT_FILE("program.mem")) u_core (
    .clk      (clk),
    .reset    (reset),
    .en       (cpu_en),
    .done     (done),
    .disp_addr (disp_addr),
    .disp_data (disp_data)
);

assign led0 = done;

// ---- result capture: scan mem[203..205] through memory port B -----
reg [1:0] scan_idx;
reg [15:0] result [0:2];    // result[0]=mem[203], [1]=204, [2]=205

assign disp_addr = 8'd203 + {6'd0, scan_idx};

always @(posedge clk) begin
    if (reset) begin
        scan_idx <= 2'd0;
        result[0] <= 16'd0;
        result[1] <= 16'd0;
        result[2] <= 16'd0;
    end else begin
        result[scan_idx] <= disp_data;
        scan_idx <= (scan_idx == 2'd2) ? 2'd0 : scan_idx + 2'd1;
    end
end

```

```

// ---- display formatting -----
// digit:  7    6    5    4    3    2    1    0
// shows: 203h 203l -- 204h 204l -- 205h 205l
wire [31:0] digits = { result[0][7:0], 4'h0,
                      result[1][7:0], 4'h0,
                      result[2][7:0] };

// Note: the display driver is deliberately NOT reset -- it keeps
// scanning while BTNC holds the CPU in reset, so the dashes are
// visible for as long as the button is held.
sevenseg_driver u_disp (
    .clk      (clk),
    .digits   (digits),
    .digit_en (8'b1101_1011), // digits 5 and 2 are blank separators
    .show_dash (~done),       // dashes until the program halts
    .an       (an),
    .seg      (seg),
    .dp       (dp)
);

endmodule

```

7.11 risc_tb.v — self-checking testbench (simulation only)

```

//-----
// risc_tb.v -- self-checking testbench for the EE 5193 RISC core
// EE 5193 FPGA and HDL, Summer 2026 -- RISC project
// Sergio Arreola
//
// Runs the ten-instruction demo program on risc_core with the clock enable
// tied high (one FSM state per clock), waits for `done`, then checks
// mem[203..205] and the involved registers against the hand-calculated
// values:
//     mem[201]=25, mem[202]=35
//     r5=25, r6=35, r7=60 -> mem[203] = 60 (0x3C)
//     r8=250, r4=225      -> mem[204] = 225 (0xE1)
//     r3=30,  r2=255      -> mem[205] = 255 (0xFF)
// Prints PASS/FAIL per check and a summary. A watchdog kills the run if
// `done` never rises (e.g. a broken FSM loop).
//-----
`timescale 1ns / 1ps

module risc_tb;

    reg clk = 1'b0;
    reg reset;
    wire done;

    integer errors = 0;

    // Device under test: core only, display port parked at 0
    risc_core #(.MEM_INIT_FILE("program.mem")) dut (
        .clk      (clk),
        .reset     (reset),
        .en       (1'b1),
        .done      (done),
        .disp_addr (8'd0),

```



```

        .disp_data ()                // unused in simulation
    );

    // 100 MHz clock
    always #5 clk = ~clk;

    // ---- check helpers -----
    task check_mem;
        input [7:0]  addr;
        input [15:0] expect;
        begin
            if (dut.u_mem.ram[addr] === expect)
                $display("PASS mem[%0d] = %0d (0x%02h)",
                    addr, dut.u_mem.ram[addr], dut.u_mem.ram[addr]);
            else begin
                $display("FAIL mem[%0d] = %0d, expected %0d",
                    addr, dut.u_mem.ram[addr], expect);
                errors = errors + 1;
            end
        end
    endtask

    task check_reg;
        input [3:0]  rnum;
        input [15:0] expect;
        begin
            if (dut.u_rf.rf[rnum] === expect)
                $display("PASS r%0d = %0d", rnum, dut.u_rf.rf[rnum]);
            else begin
                $display("FAIL r%0d = %0d, expected %0d",
                    rnum, dut.u_rf.rf[rnum], expect);
                errors = errors + 1;
            end
        end
    endtask

    // ---- stimulus -----
    initial begin
        $display("=== EE 5193 RISC testbench ===");
        reset = 1'b1;
        repeat (4) @(posedge clk);
        reset = 1'b0;

        wait (done);
        repeat (2) @(posedge clk);

        $display("--- program halted at PC = %0d after %0t ---",
            dut.u_pc.pc_out, $time);

        check_reg(4'd5, 16'd25);    // LW  r5, 201
        check_reg(4'd6, 16'd35);    // LW  r6, 202
        check_reg(4'd7, 16'd60);    // ADD r7, r5, r6
        check_reg(4'd8, 16'd250);   // LI  r8, 250
        check_reg(4'd4, 16'd225);   // SUB r4, r8, r5
        check_reg(4'd3, 16'd30);    // SRA r3, r7
        check_reg(4'd2, 16'd255);   // XOR r2, r3, r4

        check_mem(8'd203, 16'd60);  // SW r7, 203
        check_mem(8'd204, 16'd225); // SW r4, 204
        check_mem(8'd205, 16'd255); // SW r2, 205
    end

```

```

        if (errors == 0)
            $display("=== ALL CHECKS PASSED ===");
        else
            $display("=== %0d CHECK(S) FAILED ===", errors);
        $finish;
    end

    // ---- watchdog -----
    initial begin
        #10000; // 10 us >> 11 instructions x 4 states x 10 ns
        $display("FAIL watchdog timeout: done never asserted");
        $finish;
    end

endmodule

```

7.12 nexys_a7_100t.xdc — Nexys A7-100T constraints

```

# nexys_a7_100t.xdc -- pin constraints for the EE 5193 RISC project
# Sergio Arreola, EE 5193 FPGA and HDL, Summer 2026
# Pin names/sites taken from the Digilent Nexys A7-100T master XDC.

## 100 MHz system clock
set_property -dict { PACKAGE_PIN E3  IOSTANDARD LVCMOS33 } [get_ports clk]
create_clock -period 10.000 -name sys_clk -waveform {0 5} [get_ports clk]

## Center pushbutton = reset
set_property -dict { PACKAGE_PIN N17 IOSTANDARD LVCMOS33 } [get_ports btnC]

## LED0 = done indicator
set_property -dict { PACKAGE_PIN H17 IOSTANDARD LVCMOS33 } [get_ports led0]

## 7-segment cathodes (active low), seg[0]=CA ... seg[6]=CG
set_property -dict { PACKAGE_PIN T10 IOSTANDARD LVCMOS33 } [get_ports {seg[0]}]
set_property -dict { PACKAGE_PIN R10 IOSTANDARD LVCMOS33 } [get_ports {seg[1]}]
set_property -dict { PACKAGE_PIN K16 IOSTANDARD LVCMOS33 } [get_ports {seg[2]}]
set_property -dict { PACKAGE_PIN K13 IOSTANDARD LVCMOS33 } [get_ports {seg[3]}]
set_property -dict { PACKAGE_PIN P15 IOSTANDARD LVCMOS33 } [get_ports {seg[4]}]
set_property -dict { PACKAGE_PIN T11 IOSTANDARD LVCMOS33 } [get_ports {seg[5]}]
set_property -dict { PACKAGE_PIN L18 IOSTANDARD LVCMOS33 } [get_ports {seg[6]}]

## Decimal point (active low)
set_property -dict { PACKAGE_PIN H15 IOSTANDARD LVCMOS33 } [get_ports dp]

## 7-segment anodes (active low)
set_property -dict { PACKAGE_PIN J17 IOSTANDARD LVCMOS33 } [get_ports {an[0]}]
set_property -dict { PACKAGE_PIN J18 IOSTANDARD LVCMOS33 } [get_ports {an[1]}]
set_property -dict { PACKAGE_PIN T9  IOSTANDARD LVCMOS33 } [get_ports {an[2]}]
set_property -dict { PACKAGE_PIN J14 IOSTANDARD LVCMOS33 } [get_ports {an[3]}]
set_property -dict { PACKAGE_PIN P14 IOSTANDARD LVCMOS33 } [get_ports {an[4]}]
set_property -dict { PACKAGE_PIN T14 IOSTANDARD LVCMOS33 } [get_ports {an[5]}]
set_property -dict { PACKAGE_PIN K2  IOSTANDARD LVCMOS33 } [get_ports {an[6]}]
set_property -dict { PACKAGE_PIN U13 IOSTANDARD LVCMOS33 } [get_ports {an[7]}]

```

```
## Configuration
set_property CFGBVS VCC0 [current_design]
set_property CONFIG_VOLTAGE 3.3 [current_design]
```

8. Simulation Results and Waveform Discussion

I ran the self-checking testbench (`risc_tb.v`) as a Vivado behavioral simulation with the clock enable tied high, so each FSM state lasts one 10 ns clock. The whole program — eleven fetch-decode-execute-update sequences counting the HALT — completes in 475 ns. The testbench waits for done, then compares every result register and the three output memory locations against the hand calculation from Section 3.6. Three captures tell the story: a full-program overview, a close-up of four back-to-back instructions mid-program, and the testbench console output.

8.1 Full-program overview

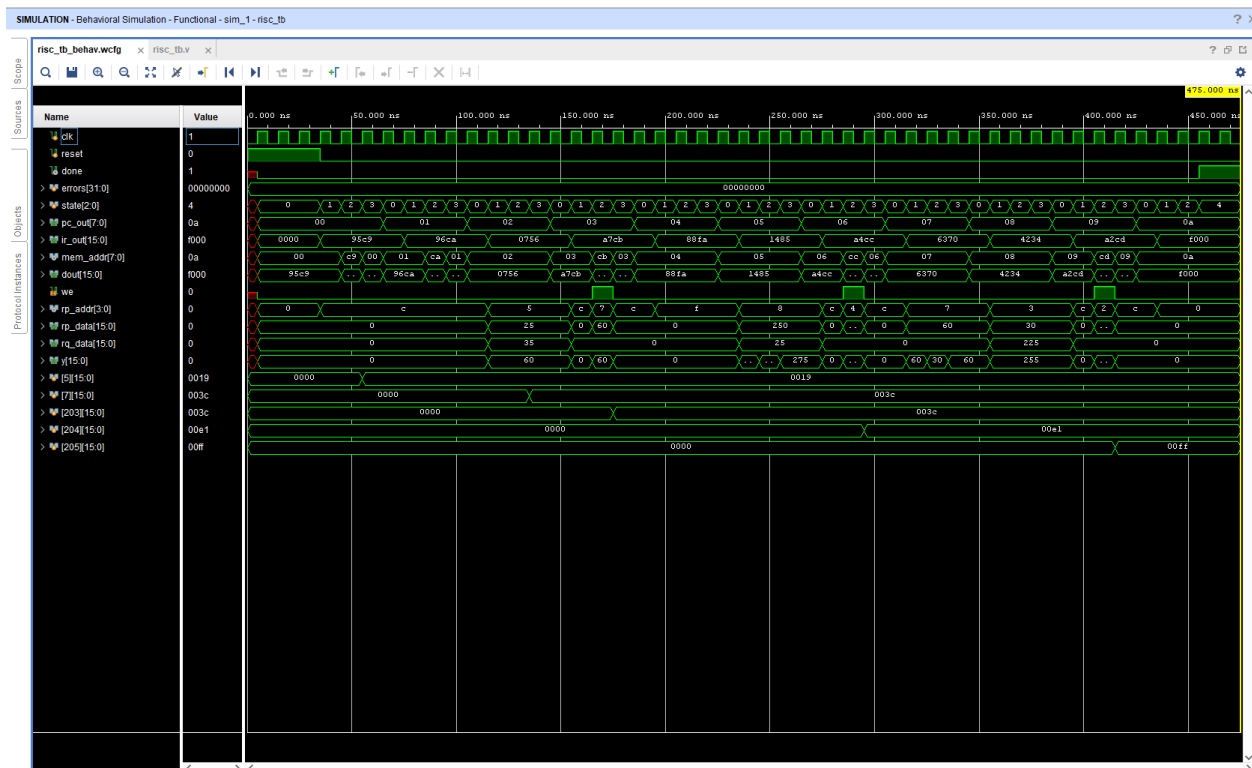


Figure 8-1: Vivado waveform, full run 0–475 ns. Signals: `clk`, `reset`, `done`, `errors`, `state`, `pc_out`, `ir_out`, `mem_addr`, `dout`, `we`, `rp_addr`, `rp_data`, `rq_data`, `y`, `rf[5]`, `rf[7]`, `ram[203]`, `ram[204]`, `ram[205]`.

One zoomed-out frame shows the entire execution. `state` ticks through 0-1-2-3 (Fetch-Decode-Execute-UpdatePC) eleven times and parks at 4 (Halt); `pc_out` staircases 00 through 0a and freezes; and `ir_out` walks through exactly the program encodings — 95c9, 96ca, 0756, a7cb, 88fa, 1485, a4cc, 6370, 4234, a2cd and finally f000, the HALT. `done` rises at 475 ns and the testbench's `errors` counter stays zero for the whole run. The unified-memory address mux is directly visible in `mem_addr`: the bus

follows the PC except during the Execute state of each load/store, where it flicks to c9, ca, cb, cc, and cd in turn — the five data addresses. The three we pulses line up exactly with ram[203], ram[204], and ram[205] stepping to 003c (60), 00e1 (225), and 00ff (255): the three results of the hand calculation landing in memory.

Individual instructions read straight off the same plot:

- During pc_out = 00 (LW r5, 201), mem_addr jumps from 00 to c9 in Execute, dout presents 0019 combinationally, and rf[5] steps to 25 on the state-exit edge.
- During pc_out = 02 (ADD r7, r5, r6), the read ports show rp_data = 25 and rq_data = 35 settled through Decode, the ALU output y shows 60, and rf[7] captures it at the end of Execute.
- During pc_out = 03 (SW r7, 203), rp_addr swings from the rs field to IR[11:8] = 7, mem_addr shows cb, we pulses, and ram[203] updates — the first visible result.

8.2 A closer look: LI → SUB → SW → SRA (180–320 ns)

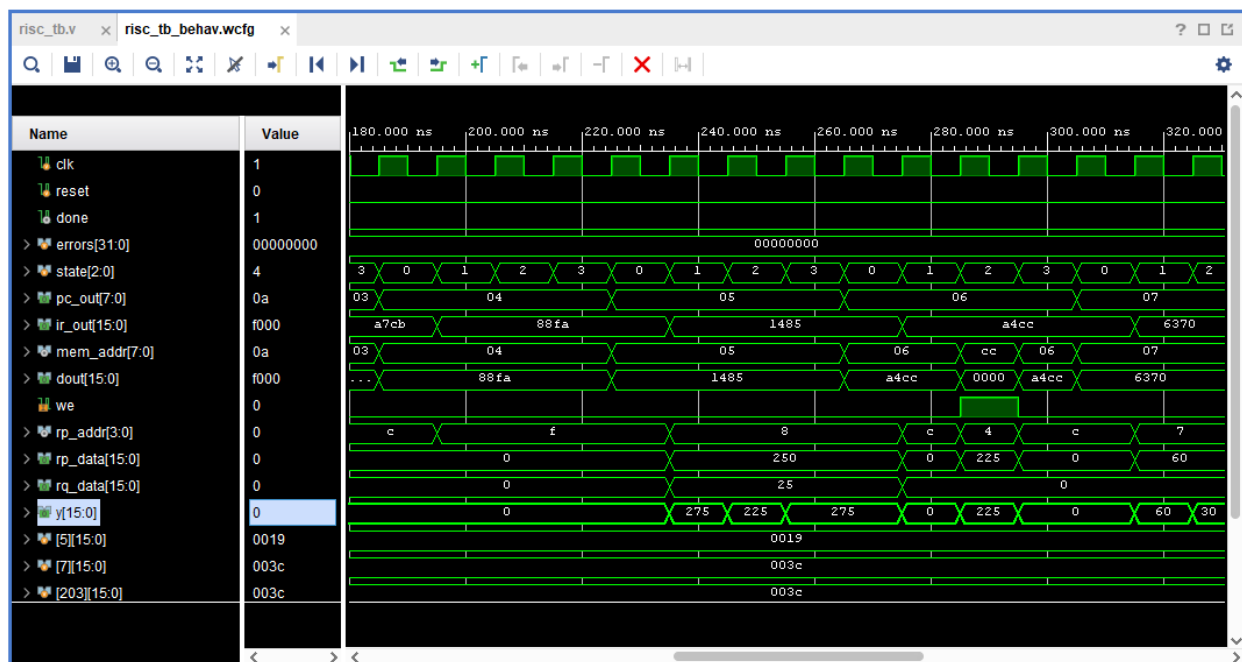


Figure 8-2: Vivado waveform, zoom of instructions 4–7 (pc_out = 04 through 07), roughly 180–320 ns — same signal set.

Zooming into the middle of the run shows four consecutive instructions of four different classes. LI r8, 250 (ir_out = 88fa) writes the zero-extended immediate; the value is visible one instruction later when SUB r4, r8, r5 reads it back as rp_data = 250 against rq_data = 25. The SUB also demonstrates the controller's per-state output discipline in a way I did not anticipate but ended up liking: the ALU output y briefly shows 275 (= 250 + 25) during Fetch, Decode, and UpdatePC, because alu_op idles at its default ADD outside the Execute state, and flips to 225 exactly when state = 2. Nothing downstream samples the ALU outside Execute, so the transient is harmless — and it is visual proof that the Execute-only strobes in the Section 6 table are doing their job. SW r4, 204 then drives

mem_addr = cc with a we pulse, and dout momentarily shows 0000 — the old contents of ram[204] appearing on the combinational read port just before the write lands — after which ram[204] steps to 00e1. Finally SRA r3, r7 starts at the right edge: rp_data = 60 in, y = 30 out, the one-bit arithmetic shift.

8.3 Testbench console output

The testbench prints one PASS/FAIL line per checked register and memory location. Output of the passing run:

```
=== EE 5193 RISC testbench ===
--- program halted at PC = 10 after 475000 ---
PASS  r5 = 25
PASS  r6 = 35
PASS  r7 = 60
PASS  r8 = 250
PASS  r4 = 225
PASS  r3 = 30
PASS  r2 = 255
PASS  mem[203] = 60 (0x3c)
PASS  mem[204] = 225 (0xe1)
PASS  mem[205] = 255 (0xff)
=== ALL CHECKS PASSED ===
```

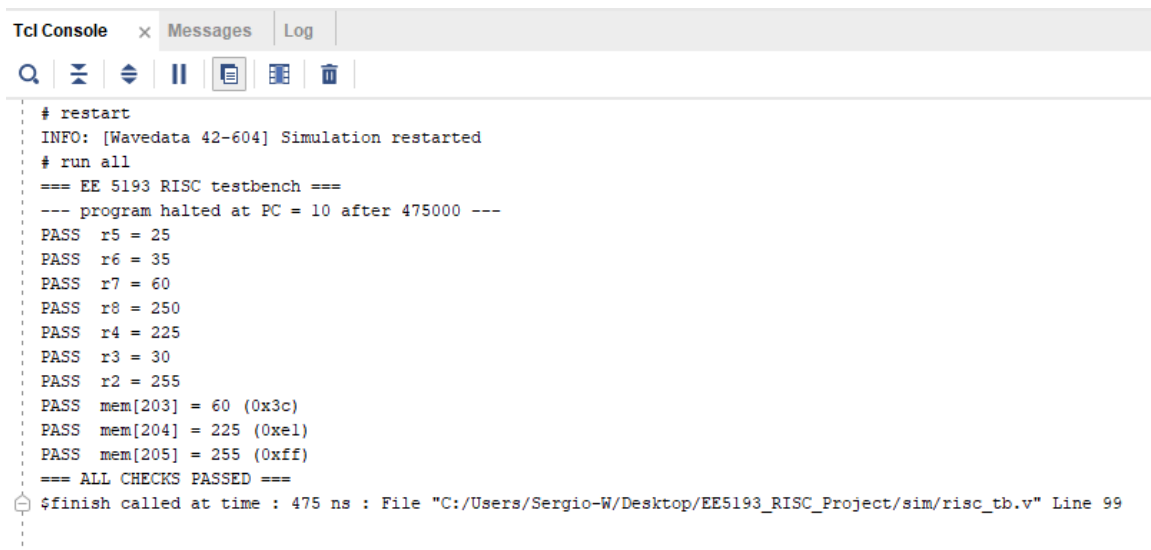


Figure 8-3: Vivado Tcl console after Run Behavioral Simulation, showing the PASS lines and “=== ALL CHECKS PASSED ===”.

9. Board Demonstration

Bring-up procedure: generate the bitstream, program the board from the Hardware Manager, and press BTNC once to reset. The program needs about 44 μ s at the 1 MHz architectural rate, so to the eye the results are instant: 3C E1 FF across the display — mem[203] = 60, mem[204] = 225, and mem[205] = 255 in hexadecimal, with the two separator digits dark and LED0 lit to indicate the HALT state was

reached. (The green DONE LED near the center of the board only means the FPGA is configured; LED0 is the processor's done flag.)

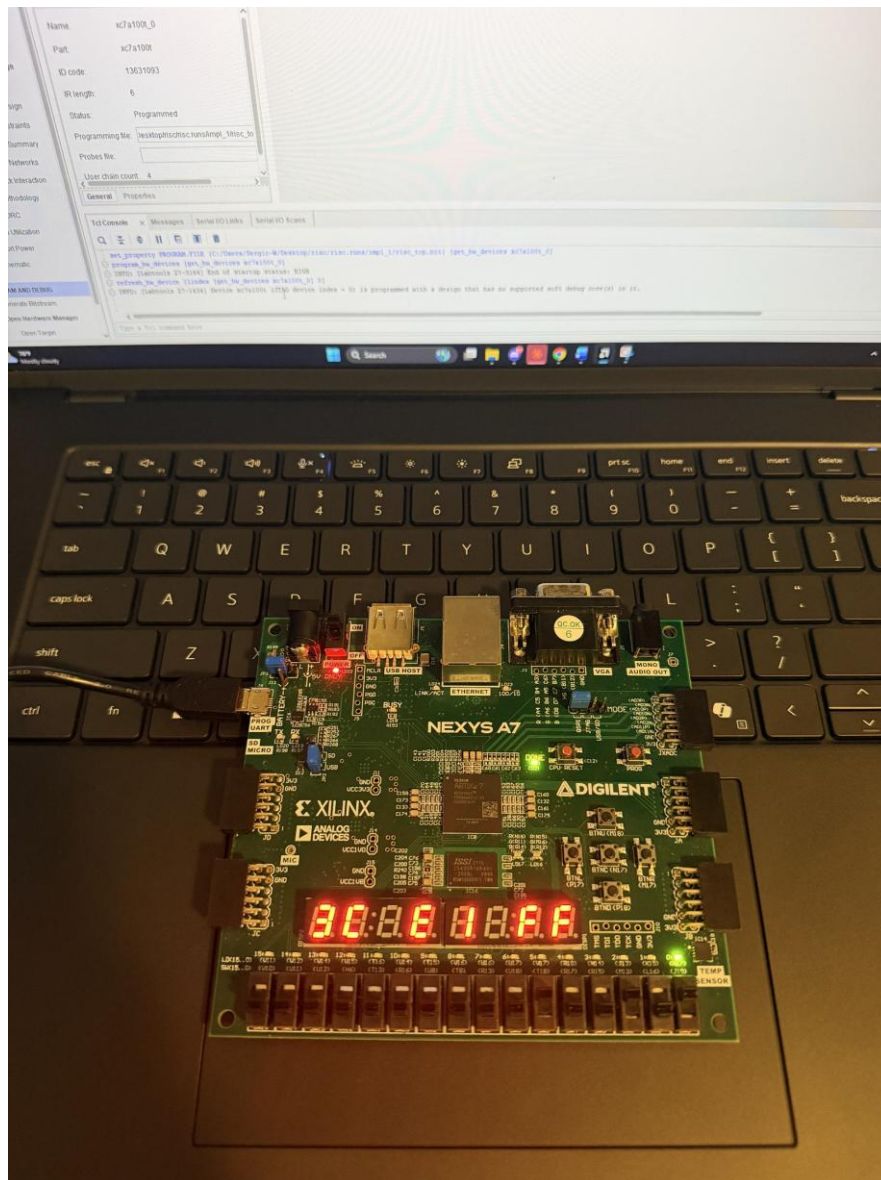


Figure 9-1: Nexys A7 running the design: display showing “3C E1 FF”, LED0 lit, Vivado Hardware Manager showing the device programmed in the background.

Holding BTNC down holds the CPU in reset: the display shows dashes (– – – –) and LED0 goes out, because done is low and the display is gated by it; releasing the button re-runs the program from scratch and the results reappear. This is the contrast shot that proves the display state is driven by the processor's status rather than frozen in the bitstream.

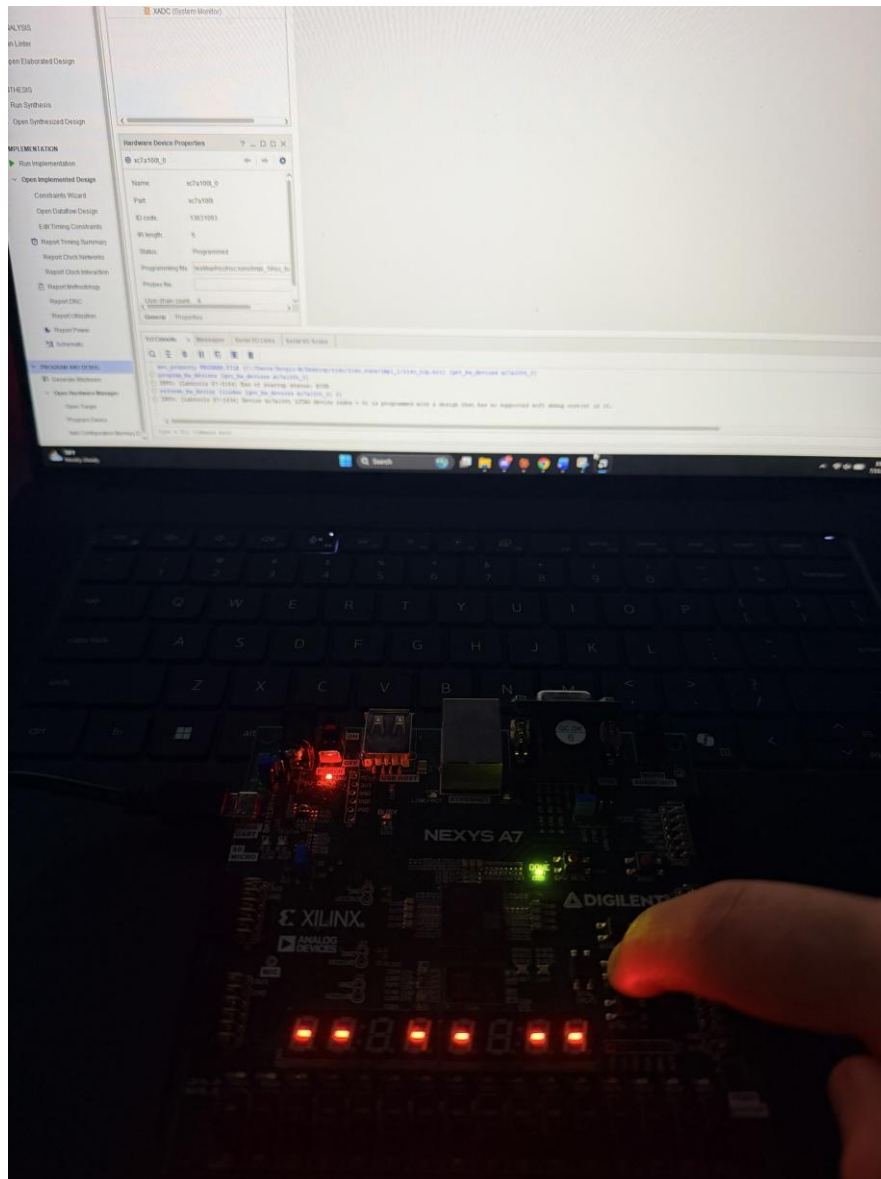


Figure 9-2: BTNC held down: display showing “-- --” with LED0 off (machine in reset, done low).

10. Problems Encountered and How I Resolved Them

10.1 The SRA encoding in the handout is inconsistent (found in simulation)

My first full-program simulation failed exactly one check: FAIL mem[205] = 225, expected 255 — the display would have shown E1 twice. Working backwards: mem[205] comes from r2, r2 comes from XOR r2, r3, r4, and the waveform showed the XOR reading rp_data = 0 for r3. r3 was never written. But the SRA result (30) had landed in r2, where the XOR then overwrote it with $0 \wedge 225 = 225$. The rd field of the handout's SRA word 0110_0010_0111_0000 is 0010 — r2, not the r3 the mnemonic SRA 3 7 claims. Since the following XOR explicitly reads r3, the mnemonic has to be right and the binary wrong, so I corrected the word to 0110_0011_0111_0000 in program.mem and re-ran: all checks passed.

(The correction is flagged in the program listing in Section 2.) Good reminder that a self-checking testbench catches what eyeballing a waveform misses — I had scrolled past that XOR several times without noticing `r3` was never written.

10.2 Registered-read memory broke the four-step model (everything off by one)

My first memory used the registered-read template so Vivado would infer block RAM. In simulation the program did nothing sensible: the first instruction executed as `0x0000` (which my decoder treats as `ADD r0, r0, r0`) and every subsequent instruction was the previous one. The cause: with a synchronous read, the data for address `PC` appears one clock **after** Fetch applies the address, so `ir_1d` was capturing the read-data register's stale contents. LW had the same one-cycle problem in its Execute state. The clean fixes are either to add a wait state to Fetch and to LW (making them two-state steps, which breaks the assignment's four-step structure) or to use a combinational read. I chose the combinational read: Vivado infers distributed LUT RAM, which at 256×16 is a trivial fraction of an XC7A100T, and the four-state execute model stays exact. The lesson I'm taking away: the BRAM-vs-LUTRAM decision is not just a resource question, it changes the cycle-level architecture.

10.3 Blocking assignment in the register file write port

Early on I had written the register file write as a blocking assignment (`rf[waddr] = wdata;`). Behavioral simulation looked fine, but it is a real race: with blocking assignments, whether another always block sampling the register file on the same edge sees the old or new value depends on simulator evaluation order, not on the design. In this design the ALU operands are sampled through combinational reads by the register write that happens on the same Execute exit edge — with the blocking write, a same-edge reader could observe the new value a delta cycle early, which is not what the flip-flop hardware will do. It surfaced as a mismatch between behavioral and post-synthesis functional simulation on the back-to-back pair `ADD r7, r5, r6 / SW r7, 203`. Changing the write to a non-blocking assignment (`rf[waddr] <= wdata;`) made both simulations agree. Rule I now follow without exception: sequential logic gets non-blocking assignments, period.

10.4 Seven-segment ghosting and phantom zeros

First hardware bring-up of the display showed two artifacts: faint copies of each digit on its neighbor (“ghosting”), and the separator digits showing dim zeros instead of being dark. The ghosting came from my original scan rate — I had grabbed counter bits `[16:14]`, and combined with the cathode pattern changing a fraction before the anode switched, each digit's segments briefly drove the next digit. Two fixes together solved it: I registered `an` and `seg` in the same always block so they change on the same edge, and slowed the scan to counter bits `[19:17]` (1.31 ms per digit, ~95 Hz frame rate — no visible flicker). The phantom zeros were a logic bug: I had blanked unused digits by feeding them nibble 0 instead of deasserting their anodes. The fix was the `digit_en` mask, which turns the anode off entirely for blanked positions. That mask then turned out to be exactly what I needed for the two dark separator columns in the `3C E1 FF` layout.

10.5 Divided clock vs. clock enable

To slow the CPU down I first did the obvious thing: a counter whose MSB toggled at ~1 MHz, used directly as the CPU clock. It worked in behavioral simulation, but Vivado flagged the divided net as a gated/derived clock (routed on fabric instead of a clock buffer), and the display logic — still on the raw 100 MHz clock — now crossed clock domains into the CPU's memory port with no synchronization, which showed up as critical warnings in the timing report. Rather than constrain a generated clock and add CDC synchronizers for a toy processor, I restructured to the standard FPGA idiom: everything clocks on the one 100 MHz clock, and the core's sequential elements are qualified by a one-cycle-in-a-hundred clock-enable pulse. All the cross-domain paths disappeared (there is only one domain), timing closed with large margin, and the CPU rate is still a one-line parameter change.

10.6 \$readmemb file not found — in synthesis but not simulation

Behavioral simulation loaded `program.mem` fine, but my first synthesis run warned that the file could not be found and happily built a memory of all zeros. On the board that meant done never rose (an all-zero memory executes `ADD r0, r0, r0` forever with the PC wrapping around), so the display sat on dashes indefinitely — my first “is the FPGA even alive?” moment of the project, resolved by reading the synthesis log instead of guessing. Simulation and synthesis resolve relative paths differently: `xsim` ran from a directory where my path happened to work, synthesis did not. The robust fix was to keep a bare filename in `$readmemb` and add `program.mem` to the Vivado project itself as a design source (it also has to be in the simulation filesset), so both tools resolve it through the project rather than the working directory. After that, both flows loaded the same image, and the post-synthesis functional simulation matched behavioral.

The same lesson then repeated in a sharper form. My original `program.mem` used `@` address directives to place the program at 0 and the operands at 201 (`@00` and `@C9` blocks), with a `//` comment per line annotating each instruction. `xsim` accepted all of it — the LRM says `@` addresses are hexadecimal regardless of the data radix, and comments are legal — but `synth_design` failed the memory module with [Synth 8-273] error in `$readmem` data: non-binary digit to `$readmemb`, absurdly followed one line later by “`$readmem` data file 'program.mem' is read successfully.” Stripping the comments didn't fix it, which is what finally pointed me at the real offender: `@C9`. Vivado synthesis parses the `@` address of a `$readmemb` file in binary, so the hex digits C and 9 are its “non-binary digit” — a straight-up LRM deviation that `xsim` doesn't share, meaning the same legal file behaves differently in the two halves of one vendor's toolchain. Rather than fight it, I flattened the image: `program.mem` now lists all 256 words in address order with no `@` jumps and no comments, and the memory's initial block is nothing but the `$readmemb` call (the explicit zero-fill loop went away since the file now covers every address). Simulation, synthesis, and my checking script all agree on that one file, and the human-readable annotated listing lives in Section 2 and Section 7.7 of this report instead of in the file.

10.7 The dash mode was unobservable — reset scope was too broad

During the board demo I held BTNC expecting to photograph the dash pattern and instead got a completely dark display with LED0 off. The logic was doing exactly what I wrote, which was not what I

meant: I had wired the synchronized reset to every module in the top level, including the 7-segment scan driver. With the driver in reset, all eight anodes are deasserted, so “machine in reset” and “display blank” were the same thing — and since the program finishes about 44 μ s after the button is released, the dashes-while-running window is far too short to see. The dash mode I had built was real but unobservable. The fix was to narrow the reset to the things that actually need one: the CPU core, the clock-enable divider, and the result-capture registers keep it, while the display driver free-runs — its outputs are a pure function of the scan counter and its current inputs, so there is no state in it worth resetting (the scan counter gets an initial value for simulation; on the FPGA the global set/reset net provides the same power-up state). Now holding BTNC shows -- -- -- with LED0 off, and releasing it snaps to 3C E1 FF — a much better demo, and a good reminder that “reset everything” is a habit, not a requirement.

11. Conclusion

The processor meets the assignment as specified: every block is its own Verilog module, the controller takes only the IR and RF_Rp_zero and walks each instruction through Fetch, Decode, Execute, and UpdatePC, and the demo program runs from the unified memory with operands 25 and 35 at locations 201/202, leaving 60, 225, and 255 in locations 203–205 and on the 7-segment display as 3C E1 FF. The self-checking testbench verifies all seven result registers and all three memory results against the hand calculation, and the design synthesizes into a single 100 MHz clock domain on the Nexys A7 in about 311 LUTs (under 0.5% of the XC7A100T, roughly half of them as distributed RAM) with no latches and timing met. Beyond the requirements, the exercise of giving RF_Rp_zero a real consumer (the JZ branch) and a defined stopping point (HALT) made the controller table and ASM-D charts feel like a complete, if small, ISA rather than a fixed-program sequencer — and the bugs in Section 10 taught me more about the simulation-to-hardware gap than the parts that worked on the first try.